

ELC 2137 Lab 05: Intro to Verilog

Maddie Vorhies

September 30, 2020

Summary

In this lab, the goal was to get familiar with Verilog and be able to produce a halfadder, fulladder, and an adder/subtractor within Verilog. For this lab it was very important to keep my files organized and adhere to the given folder structure. To begin, I created an RTL project with Basys3 as my default board. The first circuit that I created was a halfadder. For this circuit, as well as the remaining circuits, the file type is system verilog and the location is the Lab05 folder within the correct repository. To create the halfadder, I added two sources. The first source was the design source, which is what I used to build the halfadder, and the second source was the simulation source, which is what I used to test the halfadder. I also did this for the remaining circuits. The only difference is that I put each simulation source in a different folder. A halfadder consists of two inputs a and b, and two outputs c and s. I then assigned $c = a \text{ AND } b$ and $s = a \text{ XOR } b$. Now that the half adder is build, I created a simulation source that told vivado where to plug in wires and what inputs to test out. I went through the same process with the remaining circuits. Overall, my results seemed to be successful as my values matched with the expected values.

Q&A


1. What is one thing that you still don't understand about verilog?

I have trouble figuring out the error messages. When I run a simluation and it produces an error message, it takes me a while to figure out what the error actually is. Some of the errors are easy to fix, once I figure out what the porblem is. Other errors are harder to fix even after I find out what is causing the error. I feel like if I were to have a stronger base in verilog, I would either have fewer error messages or I would have a better understanding on how to fix them.


2. The results of the halfadder, fulladder, and the addsub all match the expected output results.

Results


halfadder

 

Fulladder

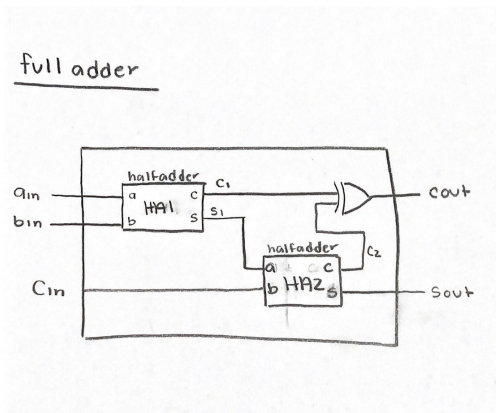

Addsub

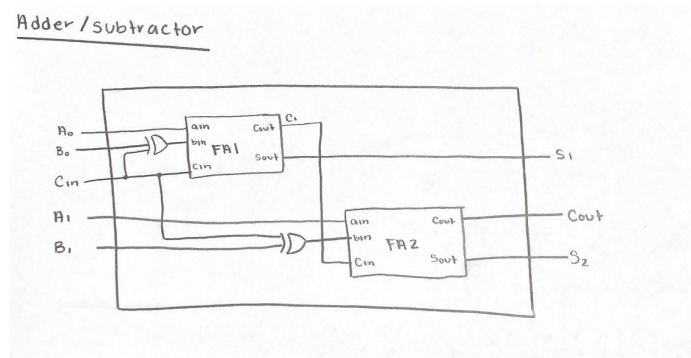

Block Diagrams

Time (ns)	0	10	20	30
a	0	1	0	1
b	0	0	1	1
c	0	0	0	1
s	0	1	1	0

 


Figure 1: Simulation Waveform and ERT of Halfadder

Time (ns)	0	10	20	30	40	50	60	70
a	0	1	0	1	0	1	0	1
b	0	0	1	1	0	0	1	1
cin	0	0	0	0	1	1	1	1
cout	0	0	0	1	0	1	1	1
sout	0	1	1	0	1	0	0	1



Figure 2: Simulation Waveform and ERT of Fulladder

Time (ns)	0	10	20	30	40	50	60	70	80	90	100	110
a1	0	0	0	0	1	1	0	0	0	0	1	1
a0	0	0	0	1	0	0	0	0	0	1	0	0
b1	0	1	1	0	0	0	0	1	1	0	0	0
b0	1	0	1	1	1	0	1	0	1	1	1	0
mode	0	0	0	0	0	0	1	1	1	1	1	1
s1	1	0	1	0	1	0	1	0	1	0	1	0
s2	0	1	1	1	1	1	1	1	0	0	0	1
cout	0	0	0	0	0	0	1	1	1	0	0	0

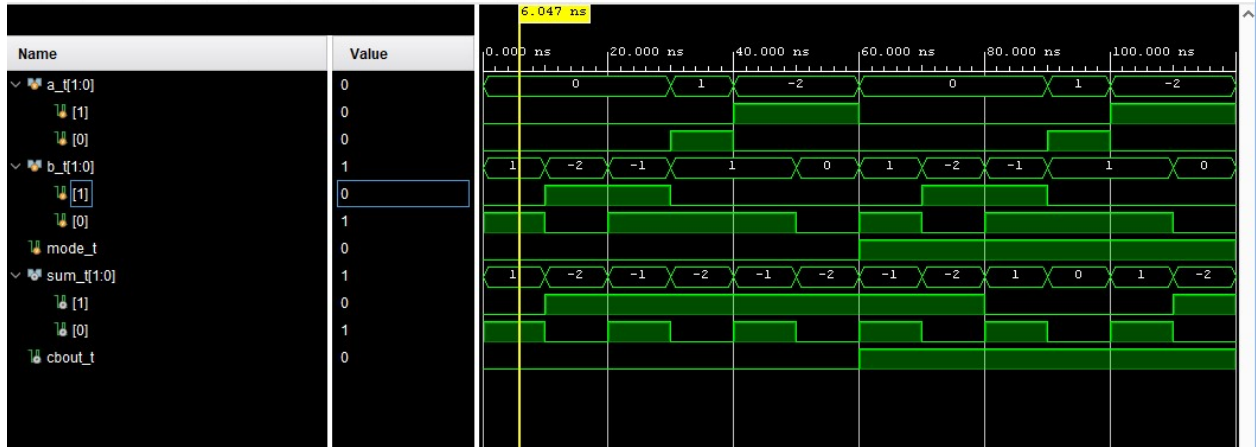


Figure 3: Simulation Waveform and ERT of AddSub

Code

```
module halfadder(  
    input a,  
    input b,  
    output c,  
    output s  
);  
  
    assign c = a & b;  
    assign s = a ^ b;  
  
endmodule  
  
module halfadder_test();  
  
    reg a1, b1;  
    wire c1, s1;  
  
    halfadder dut (  
  
        .a(a1),  
        .b(b1),  
        .c(c1),  
        .s(s1)  
    );  
  
    initial begin  
  
        a1 = 0; b1 = 0; #10;  
        a1 = 1; b1 = 0; #10;  
        a1 = 0; b1 = 1; #10;  
        a1 = 1; b1 = 1; #10;  
  
        $finish;  
  
    end  
  
endmodule  
  
module fulladder(  
    input ain,  
    input bin,  
    input cin,  
    output cout,
```

```

output sout
);

wire c1, c2, s1;

halfadder HA1 (
    .a(ain),
    .b(bin),
    .c(c1),
    .s(s1)
);

halfadder HA2 (
    .a(s1),
    .b(cin),
    .c(c2),
    .s(sout)
);

assign cout = c1 ^ c2;

endmodule

module fulladder_test();

reg ain_t, bin_t, cin_t;
wire cout_t, sout_t;

fulladder dut (
    .ain(ain_t),
    .bin(bin_t),
    .cin(cin_t),
    .cout(cout_t),
    .sout(sout_t)
);

initial begin

    cin_t = 0; bin_t = 0; ain_t = 0; #10;
    cin_t = 0; bin_t = 0; ain_t = 1; #10;
    cin_t = 0; bin_t = 1; ain_t = 0; #10;
    cin_t = 0; bin_t = 1; ain_t = 1; #10;
    cin_t = 1; bin_t = 0; ain_t = 0; #10;
    cin_t = 1; bin_t = 0; ain_t = 1; #10;
    cin_t = 1; bin_t = 1; ain_t = 0; #10;
    cin_t = 1; bin_t = 1; ain_t = 1; #10;

end

```

```

        $finish;

    end

endmodule

module addsub(
    input [1:0] a, b,
    input mode,
    output [1:0] sum,
    output cbout
);

    wire c1, c2;
    wire [1:0] b_n;

    assign b_n[0] = b[0] ^ mode;
    assign b_n[1] = b[1] ^ mode;

    fulladder FA1 (
        .ain(a[0]), .bin(b_n[0]), .cin(mode),
        .cout(c1), .sout(sum[0])
    );

    fulladder FA2 (
        .ain(a[1]), .bin(b_n[1]), .cin(c1),
        .cout(c2), .sout(sum[1])
    );

    assign cbout = c2 ^ mode;

endmodule

module addsub_test();

    reg [1:0] a_t, b_t;
    reg mode_t;
    wire [1:0] sum_t;
    wire cbout_t;

    addsub dut (

        .a(a_t),
        .b(b_t),
        .mode(mode_t),

```

```

        .sum(sum_t),
        .cbout(cbout_t)
    );

initial begin

    mode_t = 0; a_t[1] = 0; a_t[0] = 0; b_t[1] = 0; b_t[0] = 1; #10;
    mode_t = 0; a_t[1] = 0; a_t[0] = 0; b_t[1] = 1; b_t[0] = 0; #10;
    mode_t = 0; a_t[1] = 0; a_t[0] = 0; b_t[1] = 1; b_t[0] = 1; #10;
    mode_t = 0; a_t[1] = 0; a_t[0] = 1; b_t[1] = 0; b_t[0] = 1; #10;
    mode_t = 0; a_t[1] = 1; a_t[0] = 0; b_t[1] = 0; b_t[0] = 1; #10;
    mode_t = 0; a_t[1] = 1; a_t[0] = 0; b_t[1] = 0; b_t[0] = 0; #10;
    mode_t = 1; a_t[1] = 0; a_t[0] = 0; b_t[1] = 0; b_t[0] = 1; #10;
    mode_t = 1; a_t[1] = 0; a_t[0] = 0; b_t[1] = 1; b_t[0] = 0; #10;
    mode_t = 1; a_t[1] = 0; a_t[0] = 0; b_t[1] = 1; b_t[0] = 1; #10;
    mode_t = 1; a_t[1] = 0; a_t[0] = 1; b_t[1] = 0; b_t[0] = 1; #10;
    mode_t = 1; a_t[1] = 1; a_t[0] = 0; b_t[1] = 0; b_t[0] = 1; #10;
    mode_t = 1; a_t[1] = 1; a_t[0] = 0; b_t[1] = 0; b_t[0] = 0; #10;

    $finish;

end

endmodule

```