

ELC 2137 Lab 05: Intro to Verilog

Maddie Vorhies

September 30, 2020

Summary

In this lab, the goal was to get familiar with Verilog and be able to produce a halfadder, fulladder, and an adder/subtractor within Verilog. For this lab it was very important to keep my files organized and adhere to the given folder structure. To begin, I created an RTL project with Basys3 as my default board. The first circuit that I created was a halfadder. For this circuit, as well as the remaining circuits, the file type is system verilog and the location is the Lab05 folder within the correct repository. To create the halfadder, I added two sources. The first source was the design source, which is what I used to build the halfadder, and the second source was the simulation source, which is what I used to test the halfadder. I also did this for the remaining circuits. The only difference is that I put each simulation source in a different folder. A halfadder consists of two inputs a and b, and two outputs c and s. I then assigned $c = a \text{ AND } b$ and $s = a \text{ XOR } b$. Now that the half adder is build, I created a simulation source that told vivado where to plug in wires and what inputs to test out. I went through the same process with the remaining circuits. Overall, my results seemed to be successful as my values matched with the expected values.


Q&A

1. What is one thing that you still don't understand about verilog?


I have trouble figuring out the error messages. When I run a simluation and it produces an error message, it takes me a while to figure out what the error actually is. Some of the errors are easy to fix, once I figure out what the porblem is. Other errors are harder to fix even after I find out what is causing the error. I feel like if I were to have a stronger base in verilog, I would either have fewer error messages or I would have a better understanding on how to fix them.

Results


halfadder

 

Fulladder

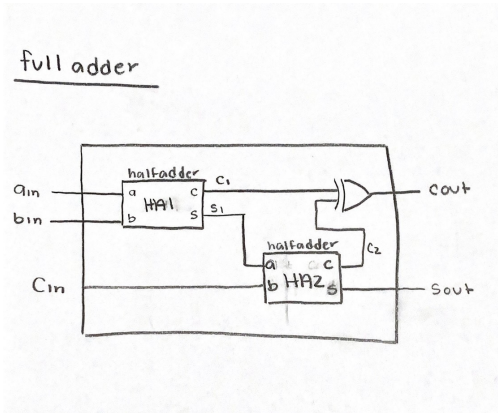

Addsub

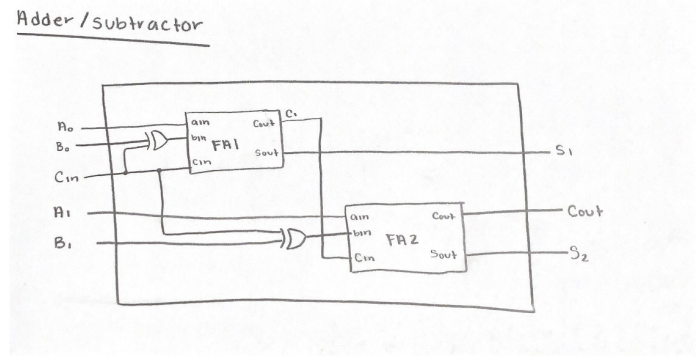

Block Diagrams

Time (ns)	0	10	20	30
a	0	1	0	1
b	0	0	1	1
c	0	0	0	1
s	0	1	1	0

 


Figure 1: Simulation Waveform and ERT of Halfadder

Time (ns)	0	10	20	30	40	50	60	70
a	0	1	0	1	0	1	0	1
b	0	0	1	1	0	0	1	1
cin	0	0	0	0	1	1	1	1
cout	0	0	0	1	0	1	1	1
sout	0	1	1	0	1	0	0	1

 


Figure 2: Simulation Waveform and ERT of Fulladder

Time (ns)	0	10	20	30	40	50	60	70	80	90	100	110
a1	0	0	0	0	1	1	0	0	0	0	1	1
a0	0	0	0	1	0	0	0	0	0	1	0	0
b1	0	1	1	0	0	0	0	1	1	0	0	0
b0	1	0	1	1	1	0	1	0	1	1	1	0
mode	0	0	0	0	0	0	1	1	1	1	1	1
s1	1	0	1	0	1	0	1	0	1	0	1	0
s2	0	1	1	1	1	1	1	1	0	0	0	1
cout	0	0	0	0	0	0	1	1	1	0	0	0

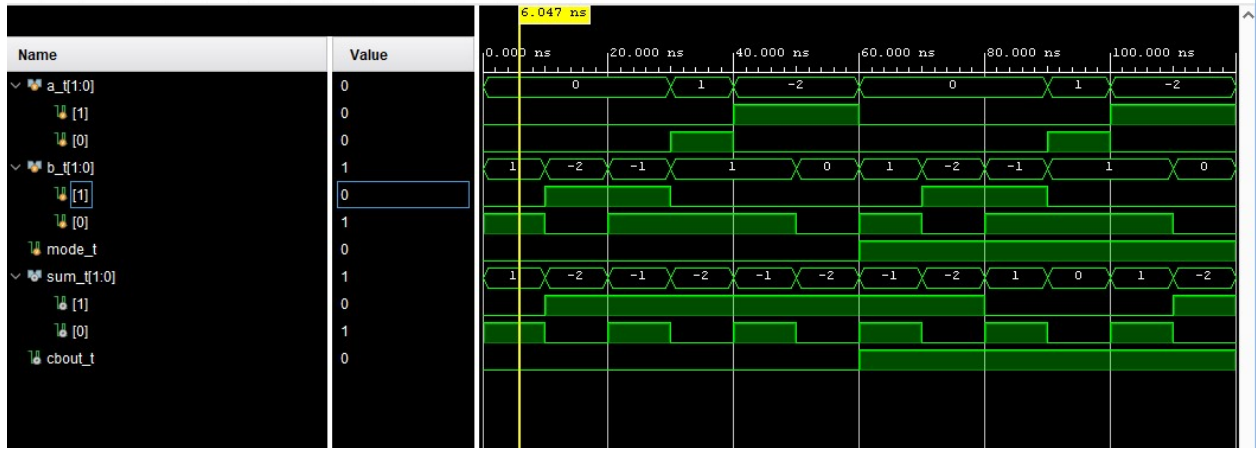


Figure 3: Simulation Waveform and ERT of AddSub

Code

```
module halfadder(  
    input a,  
    input b,  
    output c,  
    output s  
);  
  
    assign c = a & b;  
    assign s = a ^ b;  
  
endmodule  
  
module halfadder_test();  
  
    reg a1, b1;  
    wire c1, s1;  
  
    halfadder dut (  
  
        .a(a1),  
        .b(b1),  
        .c(c1),  
        .s(s1)  
    );  
  
    initial begin  
  
        a1 = 0; b1 = 0; #10;  
        a1 = 1; b1 = 0; #10;  
        a1 = 0; b1 = 1; #10;  
        a1 = 1; b1 = 1; #10;  
  
        $finish;  
  
    end  
  
endmodule  
  
module fulladder(  
    input ain,  
    input bin,  
    input cin,  
    output cout,
```

```

output sout
);

wire c1, c2, s1;

halfadder HA1 (
    .a(ain),
    .b(bin),
    .c(c1),
    .s(s1)
);

halfadder HA2 (
    .a(s1),
    .b(cin),
    .c(c2),
    .s(sout)
);

assign cout = c1 ^ c2;

endmodule

module fulladder_test();

reg ain_t, bin_t, cin_t;
wire cout_t, sout_t;

fulladder dut (
    .ain(ain_t),
    .bin(bin_t),
    .cin(cin_t),
    .cout(cout_t),
    .sout(sout_t)
);

initial begin

    cin_t = 0; bin_t = 0; ain_t = 0; #10;
    cin_t = 0; bin_t = 0; ain_t = 1; #10;
    cin_t = 0; bin_t = 1; ain_t = 0; #10;
    cin_t = 0; bin_t = 1; ain_t = 1; #10;
    cin_t = 1; bin_t = 0; ain_t = 0; #10;
    cin_t = 1; bin_t = 0; ain_t = 1; #10;
    cin_t = 1; bin_t = 1; ain_t = 0; #10;
    cin_t = 1; bin_t = 1; ain_t = 1; #10;

end

```

```

        $finish;

    end

endmodule

module addsub(
    input [1:0] a, b,
    input mode,
    output [1:0] sum,
    output cout
);

    wire c1, c2;
    wire [1:0] b_n;

    assign b_n[0] = b[0] ^ mode;
    assign b_n[1] = b[1] ^ mode;

    fulladder FA1 (
        .ain(a[0]), .bin(b_n[0]), .cin(mode),
        .cout(c1), .sout(sum[0])
    );

    fulladder FA2 (
        .ain(a[1]), .bin(b_n[1]), .cin(c1),
        .cout(c2), .sout(sum[1])
    );

    assign cout = c2 ^ mode;

endmodule

module addsub_test();

    reg [1:0] a_t, b_t;
    reg mode_t;
    wire [1:0] sum_t;
    wire cout_t;

    addsub dut (

        .a(a_t),
        .b(b_t),
        .mode(mode_t),

```

```

        .sum(sum_t),
        .cbout(cbout_t)
    );

initial begin

    mode_t = 0; a_t[1] = 0; a_t[0] = 0; b_t[1] = 0; b_t[0] = 1; #10;
    mode_t = 0; a_t[1] = 0; a_t[0] = 0; b_t[1] = 1; b_t[0] = 0; #10;
    mode_t = 0; a_t[1] = 0; a_t[0] = 0; b_t[1] = 1; b_t[0] = 1; #10;
    mode_t = 0; a_t[1] = 0; a_t[0] = 1; b_t[1] = 0; b_t[0] = 1; #10;
    mode_t = 0; a_t[1] = 1; a_t[0] = 0; b_t[1] = 0; b_t[0] = 1; #10;
    mode_t = 0; a_t[1] = 1; a_t[0] = 0; b_t[1] = 0; b_t[0] = 0; #10;
    mode_t = 1; a_t[1] = 0; a_t[0] = 0; b_t[1] = 0; b_t[0] = 1; #10;
    mode_t = 1; a_t[1] = 0; a_t[0] = 0; b_t[1] = 1; b_t[0] = 0; #10;
    mode_t = 1; a_t[1] = 0; a_t[0] = 0; b_t[1] = 1; b_t[0] = 1; #10;
    mode_t = 1; a_t[1] = 0; a_t[0] = 1; b_t[1] = 0; b_t[0] = 1; #10;
    mode_t = 1; a_t[1] = 1; a_t[0] = 0; b_t[1] = 0; b_t[0] = 1; #10;
    mode_t = 1; a_t[1] = 1; a_t[0] = 0; b_t[1] = 0; b_t[0] = 0; #10;

    $finish;

end

endmodule

```